



15122

560

I.Semester B.C.A. Examination, December 2018
(CBCS) (Fresh)
COMPUTER SCIENCE
Digital Electronics

Time : 3 Hours

Max. Marks : 70

Instruction : Answer *all* the Sections.

SECTION – A

- I. Answer **any ten** of the following. (10×2=20)
- 1) State Ohm's law.
 - 2) Define cycle and periodic time with respect to AC waveform.
 - 3) What is biasing ? Explain reverse bias.
 - 4) Differentiate Fan-In and Fan-Out.
 - 5) Define RMS value.
 - 6) Find the 2's complement of $(11010)_2$.
 - 7) Define min term and max term.
 - 8) What is AND gate ? Write its truth table and logic symbol.
 - 9) What is sequential logic circuit ? Give an example.
 - 10) What is half adder ? Write its logic circuit.
 - 11) What is conductor and insulator ?
 - 12) Define shift register.

SECTION – B

- II. Answer **any five** of the following questions. (5×10=50)
- 13) a) State and explain Norton's theorem. 5
 - b) Explain Forward and Reverse bias. 5

P.T.O.



- 14) a) What is rectifier ? Explain full wave rectifier. 5
b) Explain Kirchoff's current and voltage laws. 5
- 15) a) Differentiate intrinsic and extrinsic semiconductors. 5
b) Mention and explain briefly about the applications of diode. 5
- 16) a) State and prove Demorgan's theorem with truth table. 5
b) Simplify $AB + A(B + C) + B(B + C)$ using Boolean algebra and draw logic circuit for the simplified equation. 5
- 17) a) Simplify the SOP minterm expression $Y = \sum m(1, 5, 7, 8, 9, 13) + \sum d(3, 12)$ using K - map. 5
b) Realize all basic gates by using NOR gate. 5
- 18) a) Explain Full Adder with truth table and logic circuit. 5
b) What is multiplexer ? Explain 4×1 multiplexer. 5
- 19) a) Explain master-slave JK Flip Flop with block diagram. 5
b) Explain SISO shift register. 5
- 20) a) What is energy band ? Explain all the three energy bands. 5
b) Subtract $(29)_{10} - (7)_{10}$ using 2's complement method. 5

SECTION - B

II. Answer any five of the following questions.

- 13) a) State and explain Norton's theorem.
b) Explain Forward and Reverse bias.

(5x10=50)

5

5

P.T.O.